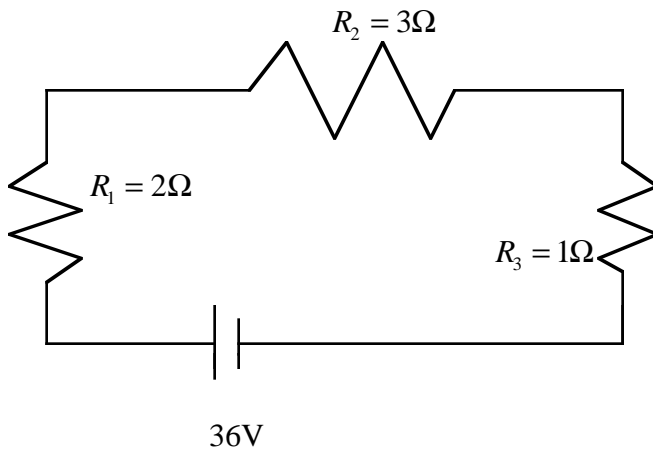


1.



Find

$$R_T = ?$$

$$I_T = ?$$

$$V_1 = ?$$

$$V_2 = ?$$

$$V_3 = ?$$


$$I_1 = ?$$

$$I_2 = ?$$

$$I_3 = ?$$

(16 pts – 2 pts each)

2.

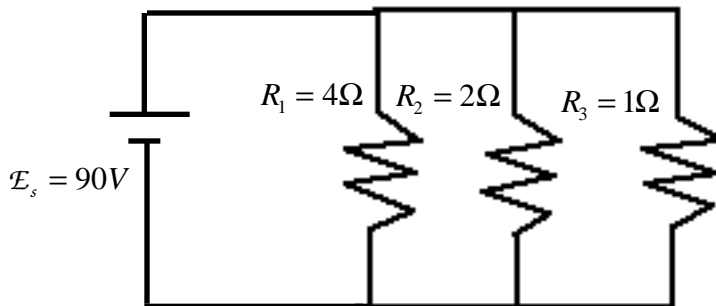

Find

$$R_T = ?$$

$$I_T = ?$$

$$V_1 = ?$$

$$V_2 = ?$$

$$V_3 = ?$$

$$I_1 = ?$$

$$I_2 = ?$$


$$I_3 = ?$$

(16 pts – 2 pts each)

3.

Find R_T or R_{EQ}

(8 pts)

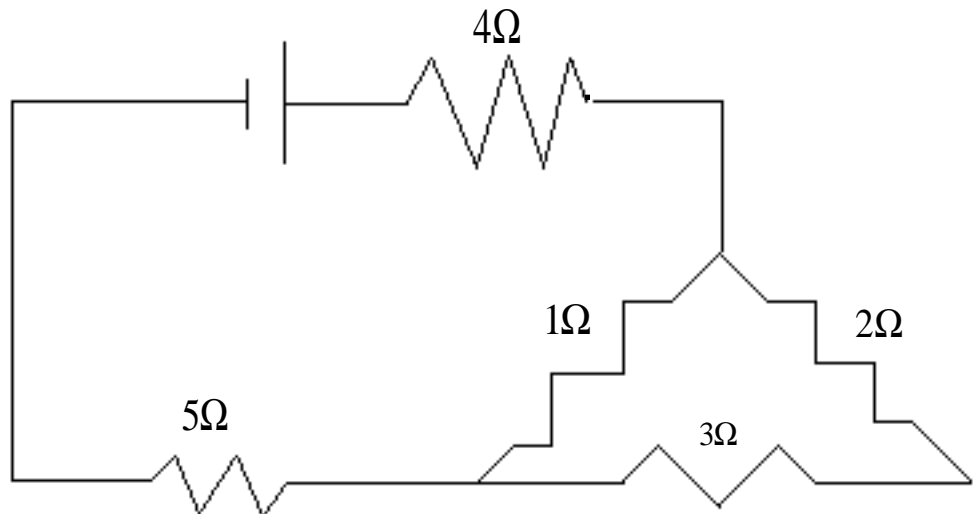


4. What is the resistance in the filament of a "100W" lightbulb rated at 120V?

Show your work.

(8 pts)

5.

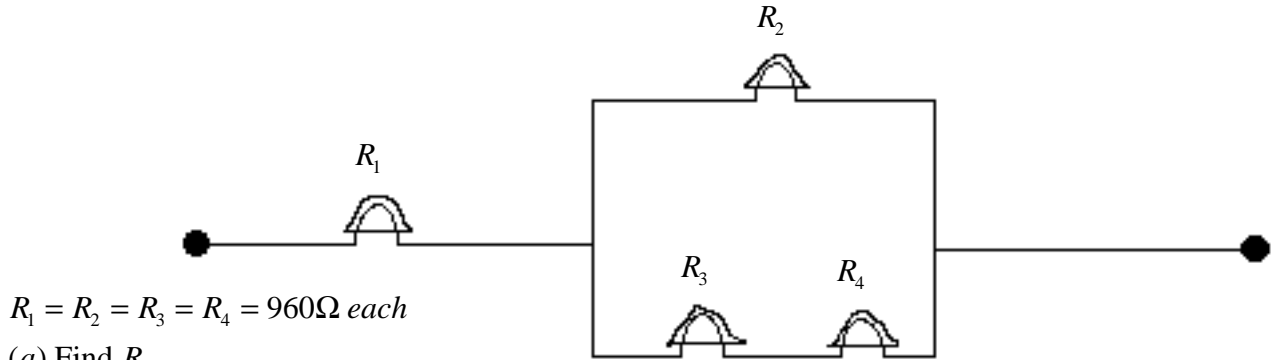

$R_1 = R_2 = R_3 = R_4 = 960\Omega$ each

- (a) Find R_T
- (b) Which bulb(s) is the brightest?
- (c) If lightbulb #4 (or R_4) is loosened from its socket, which bulb(s) is the brightest?
- (d) If lightbulb #2 is removed, which bulb is the brightest?
- (e) If lightbulb #1 is unscrewed, which bulb is brightest?

(15 pts - 3 pts each)

6. **IF** the total voltage across the above resistor combination is 120V and $R_1 = 3\Omega$, $R_2 = 6\Omega$, $R_3 = 4\Omega$, and $R_4 = 2\Omega$,

Find

(16 pts)


$R_T = ?$	$V_1 = ?$	$I_1 = ?$
$I_T = ?$	$V_2 = ?$	$I_2 = ?$
	$V_3 = ?$	$I_3 = ?$
	$V_4 = ?$	$I_4 = ?$

7. Match the following numbers with one letter (only).

- | | |
|-----------------|---------------|
| 1. Power Supply | a. flow rate |
| 2. Resistance | b. energy |
| 3. Voltage | c. friction |
| 4. Current | d. water pump |
| 5. Power | e. potential |
| | f. work/time |

(15pts - 3 pts each)

8.

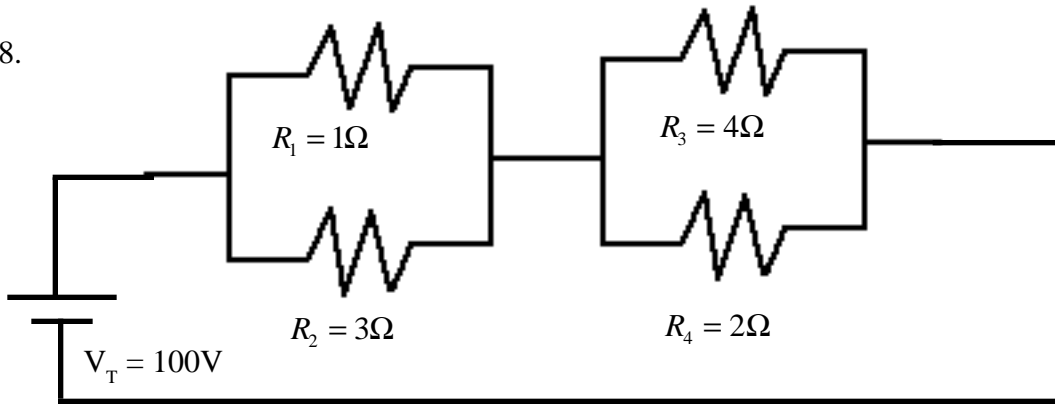


Find

$R_T = ?$	$V_1 = ?$	$I_1 = ?$
$I_T = ?$	$V_2 = ?$	$I_2 = ?$
	$V_3 = ?$	$I_3 = ?$
	$V_4 = ?$	$I_4 = ?$

(16 pts)

9. Find R_T or R_{EQ}

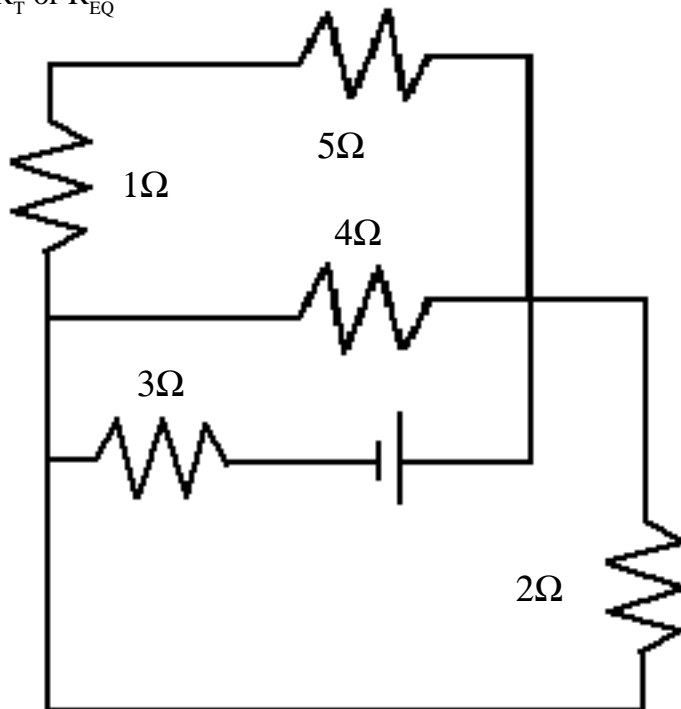

(8 pts)

10. Find R_T

(8 pts)

