

# VOLTAGE DIVIDERS


## Purpose

To study the voltage divider, learn to use a function generator, practice with the oscilloscope, and begin to work with a proto-board (breadboard).

## Introduction

Most electronic devices require a variety of voltage levels for its circuitry. Rarely is the value of a given voltage appropriate for all parts of a circuit. Whether it is an AC signal level or a DC bias, the voltage usually must be raised or reduced to a desired level. The most common method of voltage reduction is by the action of a voltage divider circuit. Shown below is a simple series of 2 resistors.


Step 1

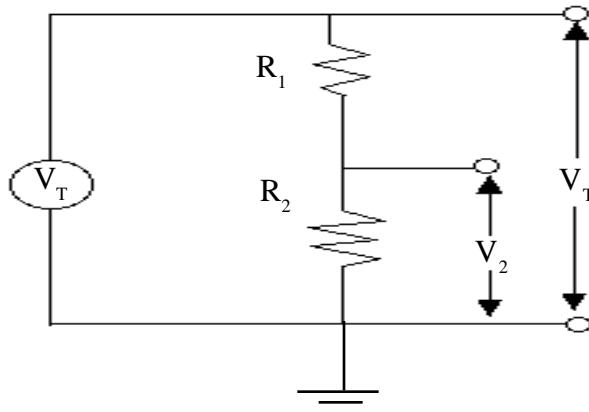

Since  $I_1 = I_2 = I_T$  we may recall that in a series circuit  $R_1 / R_2$  equals  $V_1 / V_2$ . Hence, by a suitable choice of resistors, the original or total voltage ( $V_T$ ) can be reduced to any desired voltage ( $V_1$  or  $V_2$ , or both). In its multiple resistor form, it constitutes the calibrated vertical sensitivity control of the oscilloscope. In its variable form, it constitutes the vertical and horizontal position controls. Each time you adjust the volume control of your stereo, you are altering the voltage ratio in a voltage divider circuit which in turn controls the amplitude of the amplifier output.

There are, however, some limitations. First the amount of current extracted from  $V_1$  (or  $V_2$ ) must be much less than the total current flowing through the voltage divider or the division ratio will become altered. For instance, if an external load (resistor,  $R_3$ ) uses  $V_2$ , there is a shunting effect. That is, this load and  $R_2$  would be parallel and  $1/(1/R_3 + 1/R_2)$  would have to be substituted into the resistor ratio. Thus in theory, the original resistor ratio of  $R_1 / R_2$  is only perfect if zero current is extracted using  $V_2$ . In practice, a rule of thumb states that the voltage divider is valid if less than 10% of the resistor current is diverted into an external load. Consider  $R_3$  as the external load using  $V_2$ ;

Step 2

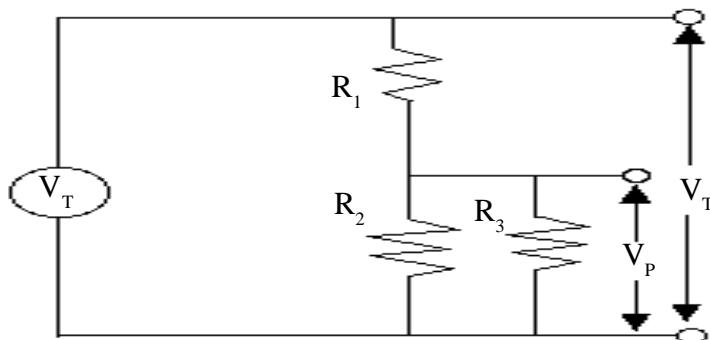

A second limitation of the divider is more subtle. For AC signals, the voltage divider action is not only due to resistance, but must also include any reactance which may be due to capacitance. This can be particularly troublesome at high frequencies and at large ratios. The effects of this AC limitation is demonstrated in step 3.

**Procedure**


**Step 1** See the diagram on the previous page. Connect two unequal resistors in series. (Use resistors from  $1\text{k}\Omega$  to  $50\text{k}\Omega$  with the same third color band. We don't want to make the resistor ratio too large.) Apply a signal of a little more than 1kHz frequency and adjust the output to a 5-15V peak-to-peak voltage ( $V_{pp}$ ). Connect this signal to the two series resistors. Use the oscilloscope to measure  $V_2$  and  $V_T$ . Calculate  $V_1$ . Note that the scope cannot measure  $V_1$  directly because both the scope and the function or signal generator have one terminal connected to the chassis and, therefore, to the grounding plug on the AC line cords. This limitation due to common grounds is ubiquitous when using test equipment. Always be aware of common ground problems. Record the values of  $R_1$  and  $R_2$ . Compare the voltage ratio with the resistor ratio using:

$$\frac{|N_1 - N_2|}{\frac{N_1 + N_2}{2}} \times 100 = \text{_____ \% deviation}$$

Where  $N_1$  and  $N_2$  are the two ratios being compared.

**Step 2** Leave  $R_1$  and  $R_2$  as before, connect a third resistor  $R_3$  in parallel with  $R_2$  as shown on the previous page. Think of  $R_3$  as an external load resistor in parallel to  $R_2$ . Measure  $V_T$  and  $V_p$  as before. Record the values of the three resistors. Calculate  $R_p$  for the parallel combination of  $R_2$  and  $R_3$ . Again compare the voltage ( $V_1 / V_p$ ) and resistor ( $R_1 / R_p$ ) ratios and calculate % deviation.

**Step 3(a)** Repeat step 1 with  $R_4$  ( $100\text{k}\Omega$  to  $600\text{k}\Omega$ ) but  $R_5$  ( $100\Omega$  to  $300\Omega$ ). Connect  $R_5$  (as the lower resistor) to ground. In this case,  $R_4 \gg R_5$  and hence the measurement of  $V_T$  and  $V_5$  will require a wide range of values for the vertical(voltage) sensitivity selector of the scope. Notice the noise level visible when measuring  $V_5$ . Record the resistor values.

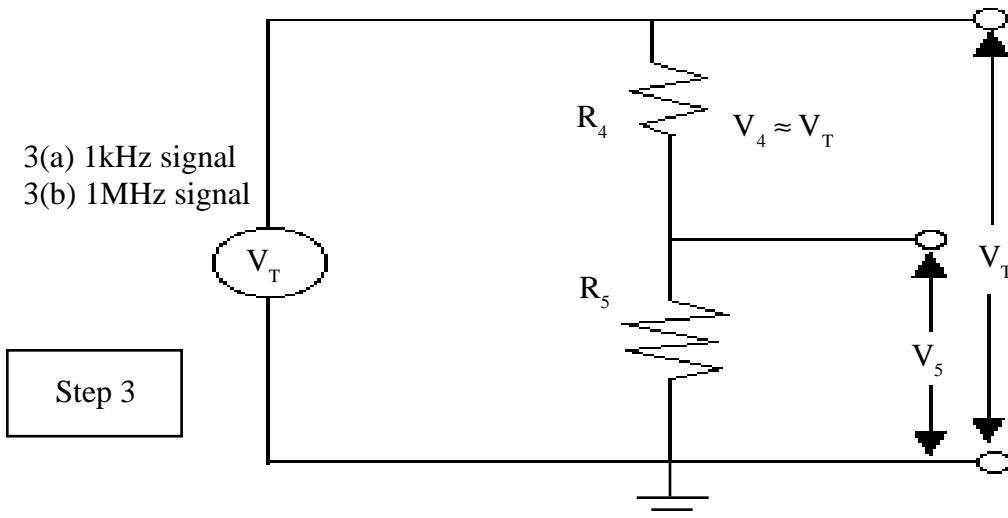

**Step 3(b)** Repeat 3(a) using a frequency greater than 1MHz.

# VOLTAGE DIVIDER WORKSHEET

Name \_\_\_\_\_

Period \_\_\_\_\_

Put all answers in decimal form.

Step 1 Series Divider

$$V_T = \text{_____} V \quad V_2 = \text{_____} V \quad R_1 = \text{_____} \Omega \quad R_2 = \text{_____} \Omega$$

$$V_1 = \text{_____} V \quad V_1 / V_2 = \text{_____} \quad R_1 / R_2 = \text{_____}$$

$$\left| \frac{\text{_____} - \text{_____}}{\text{_____}} \right| \times 100 = \text{_____} \% \text{ deviation}$$

Step 2 Parallel Divider

$$V_T = \text{_____} V \quad V_p = \text{_____} V$$

$$R_1 = \text{_____} \Omega \quad R_2 = \text{_____} \Omega \quad R_3 = \text{_____} \Omega \quad R_p = \text{_____} \Omega$$

$$V_1 = \text{_____} V \quad V_1 / V_p = \text{_____} \quad R_1 / R_p = \text{_____}$$

$$\left| \frac{\text{_____} - \text{_____}}{\text{_____}} \right| \times 100 = \text{_____} \% \text{ deviation}$$

Step 3(a) Series Divider ( $R_4 \gg R_5$ ) with f around 1kHz.

$$V_T = \text{_____} V \quad V_5 = \text{_____} V \quad R_4 = \text{_____} \Omega \quad R_5 = \text{_____} \Omega$$

$$V_4 = \text{_____} V \quad V_4 / V_5 = \text{_____} \quad R_4 / R_5 = \text{_____}$$

$$\left| \frac{\text{_____} - \text{_____}}{\text{_____}} \right| \times 100 = \text{_____} \% \text{ deviation}$$

Step 3(b) Series Divider ( $R_4 \gg R_5$ ) with f around 1MHz.

$$V_T = \text{_____} V \quad V_5 = \text{_____} V \quad R_4 = \text{_____} \Omega \quad R_5 = \text{_____} \Omega$$

$$V_4 = \text{_____} V \quad V_4 / V_5 = \text{_____} \quad R_4 / R_5 = \text{_____}$$

$$\left| \frac{\text{_____} - \text{_____}}{\text{_____}} \right| \times 100 = \text{_____} \% \text{ deviation}$$

Instructor's verification for extra credit \_\_\_\_\_